

Total No. of Questions : 8]

SEAT No. :

P4010

[Total No. of Pages : 2

[5155] - 258

M.E. (E & T/C) (VLSI & Embedded Systems)

DIGITAL CMOS DESIGN

(2013 Pattern)

Time : 3 Hour]

[Max. Marks : 50

Instructions to the candidates :

- 1) Answer any five questions.
- 2) Assume suitable data, if necessary.
- 3) Neat diagram must be drawn wherever necessary.
- 4) Use of non programmable pocket calculator is allowed.

Q1) a) Explore various wiring parasitics in detail. What are its effects on performance of the circuit? How to take care of them? [5]

b) What is SPICE? Explore SPICE model for enhancement type MOFET device in detail. [5]

Q2) a) Starting with derivation for power dissipation, explain its relation with the propagation delay of CMOS circuit. [5]

b) Explore cross talk & causes of it. What are solutions while design? [5]

Q3) a) Starting with different operating regions of MOSFET, explore equivalent circuits along with parasitics. [4]

b) Draw layout view & cross section of CMOS Inverter. Mention dimensions. [4]

c) Write note on interconnects. [2]

Q4) a) What is need of logical efforts? What are the techniques involved? How does it lead to optimization of CMOS circuit? [4]

b) Explain the delay estimation techniques in detail. Give suitable example. [4]

c) What are the advantages of transistor sizing? [2]

P.T.O.

- Q5)** a) With the help of Voltage Transfer Characteristics of CMOS Inverter, explain overall threshold & cares to be taken for symmetry. [4]
b) Design D flip flop using transmission gates. What are limitations? [4]
c) What is meant by active area on chip? Give example. [2]

- Q6)** a) Draw FSM diagram for coffee vending machine. Write HDL code. [4]
b) Design CMOS logic for $F = A + BCD$. Compare with other methods with respect to area on chip. [4]
c) Write note on metastability. [2]

- Q7)** a) Explore dynamic circuits in detail. [4]
b) What is need of NORA logic? Explain operation of such typical logic. [4]
c) What is effect of lowering threshold voltage of MOSFET on speed? Explain. [2]

- Q8)** a) Explore high speed design techniques in detail. [4]
b) What is necessity of sense amplifier circuit? With the help of diagram, explain the operation of such typical circuit. [4]
c) Write note on static CMOS. [2]

▽▽▽▽