

Total No. of Questions : 8]

SEAT No. :

P3595

[Total No. of Pages : 2

[5152]-136

S.E.(Electronics/Electronics & Telecommunication)

INTEGRATED CIRCUITS (Semester -II)

(2012 Pattern)

Time : 2 Hours]

[Maximum Marks : 50

Instructions to the candidates:

- 1) Answer Q1 or Q2, Q3 or Q4, Q5, or Q6 and Q7 or Q8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Use of electronic pocket calculator is allowed.
- 5) Assume suitable data, if necessary.

**Q1)** a) Derive the expression for  $I_{CQ}$  and  $V_{CEQ}$  for dual input balanced output difference amplifier using r-parameters. [6]

b) Define and explain following terms with respect to Op-Amp: slew Rate, input Bias Current & input offset voltage. [6]

OR

**Q2)** a) What is the need of frequency compensation? Explain dominant pole method of external frequency compensation. [6]

b) With neat diagram explain block diagram of Op-Amp and function of each block. [6]

**Q3)** a) What are the problems associated with the ideal differentiator? Draw neat circuit diagram of practical differentiator and explain its operation with its frequency response. [6]

b) Draw and explain Non inverting amplifier using Op-amp. Derive the expression for its output voltage. [6]

P.T.O

OR

**Q4)** a) Explain the necessity of Precision rectifier and explain the operation of half wave precision rectifier with neat circuit diagram. [6]

b) Draw and explain operation of inverting Schmitt trigger using Op-amp with neat waveforms. [6]

**Q5)** a) With the help of neat diagram explain the operation of Weighted binary resistor type of DAC. [7]

b) Draw neat diagram and V to I convertor with floating load and explain its operation. [6]

OR

**Q6)** a) Calculate output voltage of 8 bit DAC for digital input 10000000, 11111111 & 11110000 with reference voltage of 5V. [6]

b) With the help of neat diagram explain the operation of Flash type ADC. [7]

**Q7)** a) Draw and explain circuit of Frequency synthesizer using PLL. [7]

b) Draw neat diagram and explain three terminal adjustable voltage regulator with expression for output voltage. [6]

OR

**Q8)** a) Explain operation of PLL with the help of neat block diagram. Define the terms Lock range and capture range. [7]

b) Explain three terminal positive voltage regulator with typical circuit diagram. What are various output voltages available from such different ICs? [6]

