

Total No. of Questions—8]

[Total No. of Printed Pages—4

Seat No.	
-------------	--

[4857]-1042

S.E. (E & TC/Electronics) (I Sem.) EXAMINATION, 2015

ELECTRONIC DEVICES AND CIRCUITS

(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Attempt Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,
Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Use of calculator is allowed.

(v) Assume suitable data, if necessary.

1. (a) State and explain three stability factors. [6]

(b) Consider single stage CE amplifier with $R_s = 1 \text{ k}\Omega$,
 $R_1 = 50 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_C = 2 \text{ k}\Omega$, $R_L = 2 \text{ k}\Omega$, $h_{fe} = 50$,
 $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 25 \text{ } \mu \text{ Amp/V}$, $h_{ie} = 1.1 \text{ k}\Omega$.

Calculate : A_i , R_i and R_0 . [6]

Or

2. (a) Explain diode compensation technique against I_{CO} . [6]

(b) Calculate A_{VS} , A_{is} & R_0 for the transistor amplifier shown
in Fig. (1) having h -parameters $h_{ie} = 1.1 \text{ k}$, $h_{fe} = 50$, h_{re}

$= 2.5 \times 10^{-4}$, $h_{oe} = \frac{1}{40 \text{ k}}$. [6]

P.T.O.

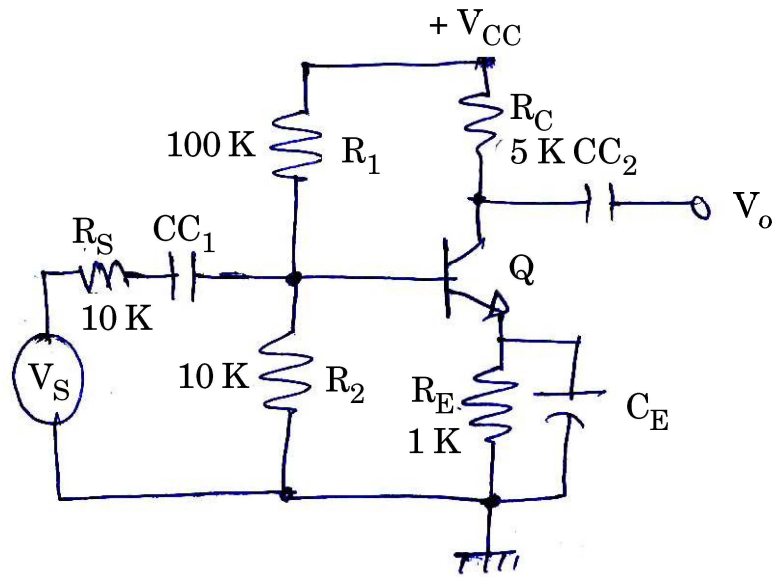


Fig. 1

3. (a) Draw and explain low frequency response of single stage RC coupled CE amplifier. [6]
- (b) Determine the frequency of Oscillation when RC phase shift oscillator has $R = 10 \text{ k}$, $C = 0.01 \mu\text{f}$ and $R_C = 2.2 \text{ k}$. Also find the minimum current gain needed for this purpose. [6]

Or

4. (a) The following measurement were taken while testing an amplifier using square wave input waveform : [6]
 - (i) for frequency of 5 kHz , $tr = 20 \mu\text{sec}$.
 - (ii) for frequency of 100 Hz , there is a sag/tilt of 1 volt in 2.5 volts .

Amplitude as observed on CRO. Determine the bandwidth of the amplifier undertest.

- (b) Draw and explain Hartley oscillator. [6]

5. (a) Draw and explain vertically oriental structure of $n-p-n$ power BJT. [6]
- (b) Class A power amplifier has zero signal collector current of 100 mA. If the collector supply voltage is 5 V, determine :
- (i) Maximum ac power output
- (ii) Power rating of transistor
- (iii) Maximum collector circuit efficiency. [7]

Or

6. (a) Draw and explain class B-push pull power amplifier. State its merits and demerits. [7]
- (b) A power amplifier supplies 3 watt to a load of 6 k Ω . The zero signal dc collector current is 55 mA and the collector current with signal is 60 mA. How much is the percentage second harmonic distortion ? [6]
7. (a) Explain the following non-ideal current voltage characteristics of MOSFET :
- (i) Finite output resistance
- (ii) Body effect
- (iii) Subthreshold conduction. [6]
- (b) Calculate the drain current and drain to source voltage of common source circuit shown in Fig. 2. Given : $V_{TN} = 1$ V, $K_n = 0.1$ mA/V². [7]

 


Fig. 2

Or

8. (a) Draw and explain constant current source biasing circuit for EMOSFET. [6]
- (b) For the circuit shown in Fig. 3 determine the small signal voltage gain. Assume parameters $V_{GSQ} = 2.12\text{ V}$, $V_{DD} = 5\text{ V}$, $R_D = 2.5\text{ k}\Omega$, $V_{TN} = 1\text{ V}$, $K_n = 0.8\text{ mA/V}^2$, $\lambda = 0.02\text{ V}^{-1}$. Assume the transistor is biased in the saturation region. [7]

 


Fig. 3