

Total No. of Questions : 8]

SEAT No. :

P4830

[Total No. of Pages : 2

[5060] - 735

M.E. (E & TC) (VLSI & Embedded Systems)

DIGITAL CMOS DESIGN

(2013 Pattern)

Time : 3 Hours]

[Max. Marks : 50

Instructions to the candidates :-

- 1) Answer any five questions.
- 2) Assume Suitable data if necessary.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Use of non programmable pocket calculator is allowed.

Q1) a) With the help of cross sectional view & equivalent circuit of MOSFET, explain various parasitic capacitances involved. Compare these capacitances for different operating regions of MOSFET. [5]

b) What is meant by technology? What is current technology? List layout design rules in detail. [5]

Q2) a) Along with the suitable example, explain RC delay model. How is it helpful to designer? [5]

b) What is significance of static & short circuit power dissipation? How to minimize them? [5]

Q3) a) Explore CMOS fabrication process in detail. [4]

b) Explain technology scaling & its types along with suitable examples.[4]

c) What is lambda parameter? Mention utility. [2]

Q4) a) Derive the expression for power delay product. What is its significance in design? What is its relation with fan out? [4]

b) Explore the methodology involved in logical efforts. Give suitable example. [4]

c) Write note on propagation delay. [2]

P.T.O.

- Q5)** a) Design CMOS logic for $Y = ABC + DEFGH$ & calculate active area on chip. [4]
b) Draw a typical logic circuit susceptible to hazards. Explain the causes of hazards & explain along with timing diagram in detail. [4]
c) What is pass transistor logic? [2]
- Q6)** a) What are merits of Transmission Gate (TG)? Design one bit latch using TGs. Compare with conventional method. [4]
b) Draw FSM diagram for 1011 Mealy sequence detector & write HDL code for it. How to make this circuit immune to metastability? [4]
c) Compare CMOS NAND & NOR in detail. [2]
- Q7)** a) Explain cascode voltage switch logic with appropriate example. [4]
b) What is need of domino logic? Explore in detail. [4]
c) What are merits of BiCMOS circuit? Give example. [2]
- Q8)** a) List the low power design techniques. Explore any one in detail. [4]
b) What materials are being used for improvement of performance? Explain in brief. [4]
c) Write note on comparison of logic families. [2]

