

Total No. of Questions : 6]

SEAT No. :

P-5387

[Total No. of Pages : 2

[6186]-513

S.E. (Electronics/Computer Engineering/E&TC) (Insem.)

DIGITAL CIRCUITS

(2019 Pattern) (Semester - III) (204182)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6.
- 2) Figures to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Use of non-programmable calculator is allowed.
- 5) Assume suitable data, if necessary.

Q1) a) Explain the following characteristics of digital IC's : [6]

- i) Fan In and Fan Out
- ii)  $I_{IL}$  and  $I_{OH}$
- iii) Propagation delay

b) Draw and explain the operation of CMOS inverter for LOW and HIGH inputs. [4]

OR

Q2) a) Draw and explain the working of 2-input CMOS NAND gate. [6]

b) Explain the following characteristics of digital IC's : [4]

- i) Noise Margin
- ii) Power Dissipation

Q3) a) Implement and explain the working of full adder using basic gates. [5]

b) Minimize the following expression using K-map and implement using logic gates : [5]

d( ) indicates don't care conditions

$$Y = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$$

P.T.O.

OR

- Q4)** a) Design 3-bit Gray to Binary code converter. [6]  
b) Design full subtractor using half subtractors. [4]

- Q5)** a) Design and implement BCD to Excess-3 code converter using logic gates. [6]  
b) Draw and explain the working of 2-input TTL NAND gate. [4]

OR

- Q6)** a) Explain the difference between current sourcing and current sinking in TTL logic. [4]  
b) Minimize the following function using Quine Mc Clusky method.[6]

$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$$

