

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

[4957]-1045

S.E. (E & TC/ Electronics) (First Sem.) EXAMINATION, 2016
DIGITAL ELECTRONICS
(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Attempt Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Assume suitable data, if necessary.

(v) Use of logarithmic tables, slide rule and electronic non programmable calculator is allowed.

1. (a) Compare TTL & CMOS logic families on the basis of :[6]
(i) Noise Margin
(ii) Fan Out
(iii) Propagation delay
(iv) Figure of merit
(v) Power supply voltage
(vi) Switching speed.
- (b) Implement the following function using single 8 : 1 Multiplexer
 $F(A,B,C,D) = \sum m(2,4,5,7,10,14)$ [6]

Or


2. (a) Design a 2 bit magnitude comparator using suitable decoder. [6]
(b) Design and explain the working of 2 input CMOS NAND Gate. [6]

P.T.O.

3. (a) Explain how shift registers are used as : [6]
 (i) Ring counter
 (ii) Twisted Ring counter.
 (b) Design and implement the following sequence generator using shift register1010..... [3]
 Design mod-5 synchronous counter using T flip-flop. [3]

Or

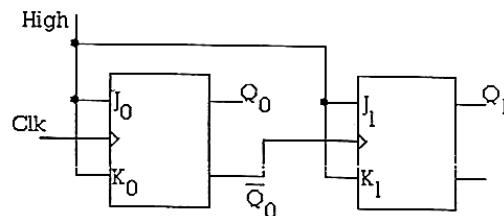4. (a) Design sequence detector to detect a sequence 1101 (Use D flip-flop and Mealy circuit) [6]
 (b) For the ripple counter shown in figure show the complete timing diagram for eight clock pulses, showing the clock, Q_0 and Q_1 waveforms. [3]



- (c) What does the word 'Finite' signify in the terms finite state machine ? State advantages and disadvantages of a finite state machine. [3]
5. (a) Generate the following Boolean functions with a PAL with 4 inputs and 4 outputs. [3]

$$Y_3 = \overline{A}BC\overline{D} + A\overline{B}C\overline{D}$$

$$Y_2 = \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}C\overline{D}$$

$$Y_1 = \overline{A}BC + A\overline{B}C + A\overline{B}\overline{C}$$

$$Y_0 = ABCD$$

- (b) Compare static RAMs and dynamic RAMs. [6]
- (c) Explain in brief the internal architecture of a PLA. [3]

Or

- 6. (a) Draw and explain 8×4 bit PROM. [6]
- (b) (i) What is PLD ?
- (ii) State *two* advantages of PLD over fixed function IC and application specific IC.
- (c) State various characteristics of memory devices and explain in brief any *two*. [3]
- 7. (a) Write a VHDL code for 4-bit ALU with minimum 4 arithmetic and 4-logical operations using behavioral modeling. [6]
- (b) Give structural description of JK flip-flop. [4]
- (c) Compare if and case statements. [3]

Or

- 8. (a) Write a VHDL code for 3-bit ripple down counter. [6]
- (b) What is difference between concurrent and sequential statements of VHDL. [4]
- (c) Give behavioral description of D flip-flop with Asynchronous Reset/Clear. [3]