

Total No. of Questions :8]

SEAT No. :

P3059

[4660]-1201

[Total No. of Pages :3

M.E. (E & TC) (VLSI & Embedded Systems)
FAULT TOLERANT SYSTEMS
(2013 Credit Pattern) (Semester - III) (604201)

Time : 3 Hours]

[Max. Marks :50

Instructions to the candidates:

- 1) *Neat diagrams must be drawn wherever necessary.*
- 2) *Assume suitable data if necessary.*
- 3) *Solve any five questions.*

Q1) a) What is binary decision diagram? Explain step by step process to draw the binary decision diagram for function $F = \bar{a} b \bar{c} + a c$. [3]

b) Define unknown logic value. Explain how to construct a truth table for 2 input XOR gate. [3]

c) Classify and define circuit simulation. Explain with neat diagram the event driven logic simulation method. [4]

Q2) a) Construct a primitive cube table for function: [3]

$$F = \bar{x}_1 \bar{x}_2 + x_1 \bar{x}_2 + \bar{x}_1 x_2 x_3$$

b) Define and explain in detail with the timing diagram, different delay models w.r.to 2 input AND gate. [4]

c) Write short note on static and dynamic hazard detection. [3]

Q3) a) State Fault Equivalence and Fault Dominance Theorem. For figure 1 determine collapse ratio by applying fault equivalence and fault dominance theorem in detail. [5]

 


Figure 1

P.T.O.

- b) State Masking Theorem. Prove that fault 'a' s-a-1 masks fault 'c' s-a-0 for the circuit as shown in figure 2. Determine the test vector for the same. [5]

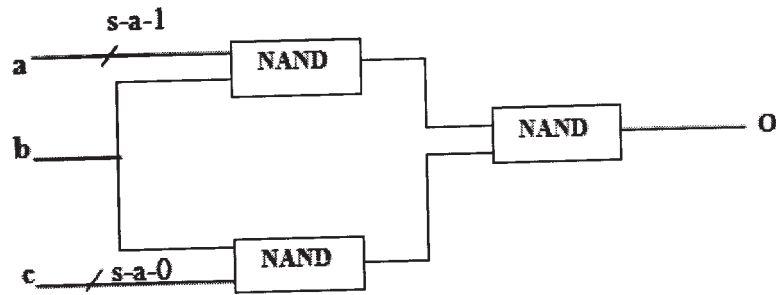


Figure 2

- Q4)** a) Explain in detail the Deductive fault simulation algorithm. [4]
 b) Define Detectability. Find test vectors that determine the OR bridging fault between input B & C in fig. 3. shown below. [4]

 


Figure 3

- c) Write short note on Wired logic and Bidirectionality. [2]
- Q5)** a) Explain single input signature analyzer to generate the output stream whose reciprocal characteristics polynomial is given by $P(X) = 1 + X^2 + X^4 + X^5$. Assume input sequence as 11110101. [5]
 b) What are the drawbacks of conventional testing approach. Classify different compression techniques. Explain One's count compression technique. [5]
- Q6)** a) What is Boundary Scan? Show a design for the boundary-Scan cell circuitry for a Bidirectional I/O pin in the IEEE 1149.1 methodology. [5]
 b) List and explain the different factors for the selection of BIST architecture. [5]

- Q7)** a) Explain any two techniques of DFT to increase controllability, observability & predictability. [4]
- b) List out the various functions carried out by BIST controller. Draw and explain with neat diagram the Generic Off-line BIST architecture. [4]
- c) Write a short note on PLA testing. [2]

- Q8)** a) Explain fault propagation using D-algorithm for the circuit shown in figure 4. [4]

 


Figure 4

- b) Explain in detail the random testing technique and suppose that the tests $W_1, W_2, W_3, W_4 = 0100, 1010, 0011, 1111$ and 0110 are chosen randomly to test the figure 5. Derive and calculate percentage of single faults detected. [4]

 


Figure 5

- c) Write short note on ATG systems. [2]

EEE