

Total No. of Questions : 8]

SEAT No. :

P2560

[Total No. of Pages : 2

M. E. (VLSI and Embedded Systems) (Semester - I)
Digital CMOS Design
(2013 Pattern)

Time : 3 Hours]

[Max. Marks : 50

Instructions to the candidates:

- 1) *Answer any five questions.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *Use of Calculator is allowed.*
- 5) *Assume Suitable data if necessary.*

- Q1)** a) Draw cross section of CMOS Inverter layout. Also draw metal, poly silicon connection diagram as top view. Show all the dimensions in terms of λ . **[5]**
- b) With the help of model of MOSFET, explore different capacitors. Give the expressions for capacitors in various regions. Which are the dominant capacitors and in which region are they developed? **[5]**
- Q2)** a) What are the types of technology scaling? What are merits and constraints? Explain in brief. **[5]**
- b) What are wiring parasitics? Explore each in detail. How to minimize these? **[5]**
- Q3)** a) Certain logic has 40 MOSFETs and each has leakage of 1 pA. If the logic operates at 2.5V, 1 GHz with load of 10 pF; compute total power dissipation. **[4]**
- b) With the help of suitable schematic, explain RC delay model. **[4]**
- c) What is short circuit dissipation? How to minimize it? **[2]**

P.T.O.

- Q4)** a) Derive the expression for Power delay product. What is the significance of PDP? [4]
b) What is need of logical efforts? Explain with suitable example. [4]
c) Explain in brief delay in multistage logic networks. [2]
- Q5)** a) Explore voltage transfer characteristics of CMOS inverter. Give the expression for propagation delay. [4]
b) Design CMOS logic for $Y = ABC + DE + FGHI$. Compute active area on chip. [4]
c) What are the merits and demerits of transmission gate? [2]
- Q6)** a) With suitable schematic, explain D-latch using transmission gate. [4]
b) Draw FSM diagram and write HDL code for 4 bit ring counter. [4]
c) Why is CMOS NAND preferred over NOR gate? [2]
- Q7)** a) Explain NORA logic with suitable example. [4]
b) What is ratioed logic circuit? Why is it needed? [4]
c) Draw and explain sense amplifier circuit. [2]
- Q8)** a) Explore domino logic with appropriate example. [4]
b) Write note on high speed designs. [4]
c) List the materials used for performance improvement. [2]

