

Total No. of Questions : 8]

SEAT No. :

P2610

[Total No. of Pages : 2

M.E. (E & TC) (VLSI and Embedded Systems)

ANALOG CMOS DESIGN

(2013 pattern) (Semester-II) (504207)

Time : 3 Hours]

[Max. Marks : 50

Instructions to the candidates:

- 1) *Answer any five questions.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *Use of Calculator is allowed.*
- 5) *Assume Suitable data if necessary.*

Q1) a) With the help of suitable schematic and necessary expressions, explore MOSFET as switch, diode and active resistor. **[5]**

b) Draw typical circuit diagram for band gap reference and derive the expression for output voltage. **[5]**

Q2) a) Draw current sink/source. How to improve output resistance? Derive the expression. **[5]**

b) Design cascode current mirror for i_{OUT} of 10 μA . Assume suitable data. **[5]**

Q3) a) For active load inverter, derive the expressions for $V_{OUT\ max}$, $V_{OUT\ min}$, A_v and r_{OUT} . **[4]**

b) Carry out large signal analysis of CMOS differential amplifier and find out $V_{OUT\ max}$, $V_{OUT\ min}$ and ICMR. **[4]**

c) What are limitations/constraints due to output offset voltage of CMOS Opamp? **[2]**

Q4) a) Compare active load, current source and push pull inverters w.r.t. V_{OUT} , A_v , r_{OUT} and bandwidth. **[4]**

b) Carry out small signal analysis of CMOS differential amplifier and derive A_v , r_{OUT} , CMRR and bandwidth. **[4]**

c) Which are dominant noise in CMOS Opamp? List the techniques to reduce these noise. **[2]**

P.T.O.

- Q5)** a) Design multistage amplifier for $A_v = 40$ dB and bandwidth = 100 MHz. Comment on r_{OUT} . Assume suitable data. [4]
 b) Explore open circuit time constant method analytically in detail. [4]
 c) List assumptions and limitations of short circuit time constant method. [2]
- Q6)** a) How to use zeros as bandwidth enhancer? Explain shunt peaking in amplifier. Give the expression for extended bandwidth. [4]
 b) What are the constraints on input admittance of tuned amplifier? Explore unilateralization and neutralization in short. [4]
 c) What are techniques to improve bandwidth? [2]
- Q7)** a) What is power constrained noise optimization? Explore with necessary expressions. [4]
 b) Draw schematic for any one type of CMOS mixer and explain with analysis. [4]
 c) What are spurs in mixer? [2]
- Q8)** a) Draw single ended LNA. Mention the drawbacks and show how these are overcome in differential LNA? [4]
 b) Brief advanced trends in RF chip design. [4]
 c) Define conversion gain and noise figure w.r.t. mixer. [2]

●●●●●