

Total No. of Questions—8]

[Total No. of Printed Pages—2

Seat No.	
-------------	--

[5559]-133

S.E. (E & TC/Electronics) (I Sem.) EXAMINATION, 2019
ELECTRONIC DEVICES AND CIRCUITS
(2012 PATTERN)

Time : Two Hours

Maximum Marks : 50

N.B. :— (i) Attempt Q. No. 1 or 2, Q. No. 3 or 4, Q. No. 5 or 6, Q. No. 7 or 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Use of Calculator is allowed.

(v) Assume suitable data, if necessary.

1. (a) Draw a neat circuit diagram of Self-bias circuit. Derive the expression for V_{CEQ} and I_{CQ} . [6]
- (b) The transistor is connected in CE amplifier with bypassed R_E has $R_1 = 50 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_C = 1 \text{ k}\Omega$, $R_S = 1 \text{ k}\Omega$, $R_L = 10 \text{ kW}$. Also h -parameters $h_{ie} = 1.1 \text{ k}\Omega$, $h_{fe} = 50$, $h_{oe} = 24 \text{ }\mu\text{A/V}$, $h_{re} = 2.5 \times 10^{-4}$. Determine the value of A_v , A_{vs} , A_l , R_i' . [6]

Or

2. (a) Explain in detail the three factors which contribute to thermal instability ? [6]
- (b) Define hybrid parameters of CE configuration of BJT with formulas. Draw its hybrid equivalent circuit for CE configuration. [6]
3. (a) Define and derive expression for f_α , f_β and f_T . [6]
- (b) Draw and explain the circuit diagram of Hartley Oscillator using BJT and give expression for frequency of oscillation. [6]

P.T.O.

Or

4. (a) Draw and explain CE short circuit current gain using Hybrid- π model. [6]
(b) In Hartley Oscillator $L_1 = 15$ mH, $C = 50$ pF. Calculate L_2 , for frequency of 168 kHz. [6]
5. (a) Explain the following parameters of power BJT : [6]
(i) Safe operating area
(ii) Thermal resistance.
(b) Draw circuit diagram of class B push pull amplifier and explain its operation with neat waveforms. [7]

Or

6. (a) What is crossover distortion ? How is it reduced in complementary symmetry class AB amplifier ? [6]
(b) A class B push pull amplifier is supplied with $V_{CC} = 12$ V and load resistance of 5Ω . If input is sinusoidal, calculate : (i) Maximum power output (ii) Power dissipation in both transistors, (iii) Power dissipation in each transistor, (iv) percentage efficiency. [7]
7. (a) Draw and explain Bi-CMOS inverter. [6]
(b) Explain various non-ideal current voltage characteristics of EMOSFET. [7]

Or

8. (a) The parameters of NMOSFET are $k = 0.2$ mA/V², $\lambda = 0.01$ V⁻¹, $V_T = 1.2$ V. Calculate output resistance for (i) $V_{GS} = 2$ V, (ii) $V_{GS} = 4$ V. [6]
(b) Draw and explain constant current source biasing circuit for EMOSFET. [7]