

Total No. of Questions : 4]

SEAT No. :

PB-132

[Total No. of Pages : 2

[6269]-346

T.E. (E&TC Engineering) (Insem)
POWER DEVICES & CIRCUITS
(2019 Pattern) (Semester - II) (304194)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) *Answer Q1 or Q2, Q3 or Q4.*
- 2) *Neat diagrams and waveforms must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *Use of nonprogrammable calculator is allowed.*
- 5) *Assume Suitable data if necessary.*

Q1) a) Draw construction diagram of power MOSFET? Explain V-I characteristics of power MOSFET. [7]

b) Draw V-I characteristics of SCR? Explain the following w.r.t. SCR & write their typical values. [8]

- i) Break over voltage
- ii) Latching current
- iii) Holding current

OR

Q2) a) Draw & explain synchronized UJT triggering circuit with suitable waveforms. [7]

b) Draw and explain gate drive circuit for IGBT. [5]

c) Compare SCR with GTO. [3]

Q3) a) What is commutation? Explain with diagram natural & forced commutation. [5]

b) Draw & explain single phase full converter for R-L load with circuit diagram and voltage & current waveforms. [10]

P.T.O.

OR

- Q4)** a) Draw & explain three phase fully controlled converter with R load with circuit diagram & waveforms. [9]
- b) A single phase semi-converter is operated from the 120V, 60Hz AC input supply. The load is resistive of 10 Ohm. If the firing angle is 30 degree. Calculate : [6]
- i) Average o/p voltage
 - ii) Average o/p current
 - iii) RMS o/p voltage
 - iv) RMS o/p current
