

Total No. of Questions : 8]

SEAT No. :

P5403

[Total No. of Pages : 2

[5562]-264

M.E. (E & TC) (VLSI & Embedded Systems)

ANALOG CMOS DESIGN

(2017 Pattern)

Time : 3 Hours]

[Max. Marks : 50

Instructions to the candidates :

- 1) Attempt any five questions.
- 2) Figures to the right in bold indicate full marks.
- 3) Assume suitable data if necessary.

**Q1)** a) How does MOSFET behave as PN diode? What are its applications? Give the expressions for its DC current and dynamic resistance. [5]

b) With the help of a diagram, explain small signal high frequency model for the MOS transistor. Also draw large signal model. [5]

**Q2)** a) Explain the effect of channel length modulation and body effect on MOSFET & show how these are accounted in basic small signal model. [4]

b) What is need of voltage/current references? Explain in detail the concept of BGR with its necessity. [4]

c) List the performance parameters of voltage reference circuits. [2]

**Q3)** a) What do you mean by large signal, small signal analysis? Draw the schematic of CMOS difference amplifier with current mirror load give the expression for G<sub>md</sub>, ICMR, CMRR and 3dB frequency. [5]

b) What are limitations/constraints due to output offset voltage of CMOS op amp. [3]

c) Which are dominant noises in CMOS Op amp? List the techniques to reduce this noise. [2]

P.T.O.

- Q4)** a) Compare Active load, Current source load and Push-pull inverter with respect to important performance parameters. [4]
- b) What is CS-CG cascode amplifier, draw its schematic and discuss its advantages/disadvantages over single stage amplifier. [4]
- c) What is effect of source degeneration resistance on the voltage gain of CS amplifier? [2]
- Q5)** a) List and explain important static and dynamic characteristics of comparator. [3]
- b) What is need of compensation in multistage amplifiers. Explain Miller Compensation in two stage CMOS Op amp. [5]
- c) How propagation delay is related with slew rate, derive the relation. [2]
- Q6)** a) Draw and Explain Following Analog Circuits (Any Two) : [5]
- i) Cascode Current mirror Source.
- ii) Single ended and double ended CMOS differential amplifiers.
- iii) CMOS Comparator.
- b) Write a note on stability of Op amp and its effect on slew rate. What are different ways to improve stability? [5]
- Q7)** a) Explain differential LNA with neat circuit diagram. [4]
- b) With the help of schematic in detail, explore the design steps of single ended LNA. [4]
- c) Explain Spurs in Mixer. [2]
- Q8)** a) How to use zeros as bandwidth enhancer? Explain shunt peaking in amplifier. Give the expression for extended bandwidth. [4]
- b) How nonlinear systems work as linear mixers. Explain square-law MOSFET mixer with neat circuits. [4]
- c) What are the techniques to improve the bandwidth? [2]

