

Total No. of Questions : 8]

SEAT No. :

**P3939**

[Total No. of Pages :2

**[5462] - 661**

**M.E. (E&TC) VLSI & Embedded Systems**

**DIGITAL CMOS DESIGN**

**(2017 Pattern) (Semester - I)**

*Time : 3 Hours]*

*[Max. Marks :50*

*Instructions of the candidates:*

- 1) *Answer any five questions.*
- 2) *Assume Suitable data if necessary.*
- 3) *Neat diagrams must be drawn wherever necessary.*
- 4) *Use of nonprogrammable calculator is allowed.*

**Q1)** a) With the help of diagram & typical dimensions, explain cross section of CMOS Inverter. Comment on the doping concentrations & poly silicon layer. **[5]**

b) What is need of technology scaling? Explain the types & their characteristics in detail. **[5]**

**Q2)** a) Derive the expression for power delay product. How is it useful to the designer? **[5]**

b) Explore multistage logic network & delays. **[5]**

**Q3)** a) Explore equivalent circuit of MOSFET. Explain the  $g_m$ ,  $C_{gs}$  & their significance. **[4]**

b) With the help of suitable diagrams, explore n-well process. **[4]**

c) What is need of transient analysis? **[2]**

**Q4)** a) Explain various RC delay models in brief. Comment on their accuracies. **[4]**

b) With the help of mathematical analysis, explain the need of transistor sizing. **[4]**

c) Write note on design margin. **[2]**

**P.T.O.**

- Q5)** a) Draw a logic circuit involving dynamic hazards & explain the waveforms. [4]  
 b) Design five input CMOS NAND & NOR gates. Compare w.r.t.area, dissipation & delay. [4]  
 c) Why hazards are not so serious in synchronous machines? [2]
- Q6)** a) Design CMOS logic for  $P = ABCDE + F + G + H$ . Comment on area & propagation delay. [4]  
 b) Draw FSM diagram & write HDL code for tea/coffee vending machine. Assume suitable data. [4]  
 c) Design 4:1 mux using transmission gates. Compare with conventional method. [2]
- Q7)** a) What are merits of differential circuits? Explore sense amplifier based circuit in detail. [4]  
 b) Compare at least three logic families in detail. [4]  
 c) Write note on techniques of low power design. [2]
- Q8)** a) What is merit of dynamic circuit? Explain with schematic. [4]  
 b) Explain in brief about materials involved in performance improvement. Give at least two examples. [4]  
 c) Write note on high speed design. [2]

@@@@@