

Total No. of Questions : 8]

SEAT No. :

P9102

[Total No. of Pages : 2

[6179]-227

S.E. (Electronics / E & TC / Computer)

DIGITAL CIRCUITS

(2019 Pattern) (Semester-III) (204182)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Solve Q.No.1 or Q.No.2, Q.No.3 or Q.No.4, Q.No.5 or Q.No.6, Q.No.7 or Q.No.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Use of Calculator is allowed.
- 5) Assume suitable data, if necessary.

Q1) a) Explain binary subtraction using 1's compliment and two's compliment method with example. [6]

b) Design and explain 3-bit parity generator circuit. [6]

c) Implement 1:8 demux using 1:4 demux. [6]

OR

Q2) a) Design and explain 2-bit comparator circuit using logic gates. [6]

b) Implement 16:1 Mux using 4:1 Mux. [6]

c) Explain Look ahead carry generator circuit. [6]

Q3) a) Explain working of SR Flip flop with neat Block diagram and truth table. [6]

b) Convert JK flip flop into D flip flop. [6]

c) Design and implement 2-bit synchronous counter using T flip flop. [5]

OR


Q4) a) Explain working of JK Flip flop with neat Block diagram and truth table. [6]

b) Convert SR flip flop into T flip flop. [6]

c) Write short note on Shift registers. [5]

P.T.O.

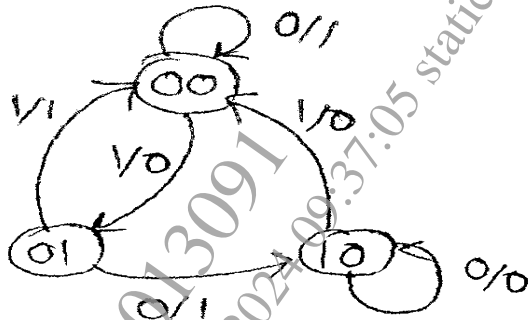- Q5) a)** Design the sequential circuit for the given state diagram using T flip flop. [9]



- b) Design and implement circuit using D flip flop to detect the following binary sequence 110. [8]
- Q6) a)** Draw ASM chart for 2 bit binary counter having enable line E such that: E=1, Count Enable and E=0, Count Disable. [9]
- b) Write short note on state reduction with suitable example. [8]
- Q7) a)** Explain the block diagram of memory unit? [9]
- b) Explain FPGA architecture. [9]
- OR
- Q8) a)** Design and implement Full Subtractor using PAL? [9]
- b) Explain CPLD architecture. [9]

