

[4760] - 1142

M.E. (E & TC) (VLSI & Embedded Systems) (Semester - II)

ANALOG CMOS DESIGN

(2013 Pattern)

Time : 3 Hours]


[Max. Marks : 50

Instructions to the candidates:

- 1) Answer any five questions.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks.
- 4) Use of Calculator is allowed.
- 5) Assume Suitable data if necessary.

SECTION - I

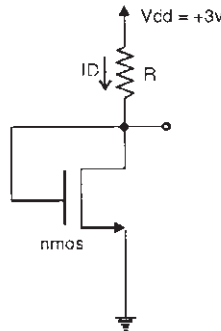
- Q1) a)** For the circuit shown in figure, Find 'R' and the d.c. voltage ' V_D '. If the drain current I_D is $80\mu A$. The NMOS transistor used have $V_t = 0.6V$, $\mu_n C_{OX} = 200\mu A/V^2$, $L = 0.8\mu m$, $W = 4\mu m$. [5]



- b)** Draw the transistorized network of Common source amplifier, Common gate amplifier and common drain amplifiers. Differentiate these amplifiers with respect to following terms, [5]
- i) Input resistance
 - ii) Output Resistance
 - iii) Intrinsic Voltage Gain


P.T.O.

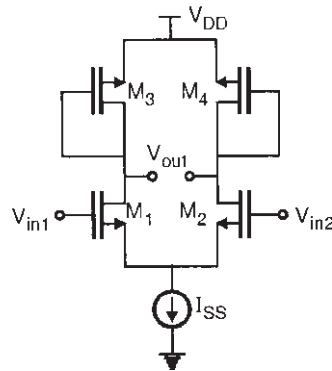- Q2) a)** Determine the voltage gain of the circuit shown in Figure. Assume $\lambda \neq 0$. Assume M_1 is identical to M_2 and M_3 is identical to M_4 . [5]



- b) Explain how CMOS inverter can be used as an amplifier. Draw the neat circuit diagram of two stage CMOS OP-Amp and explain its operation. [5]

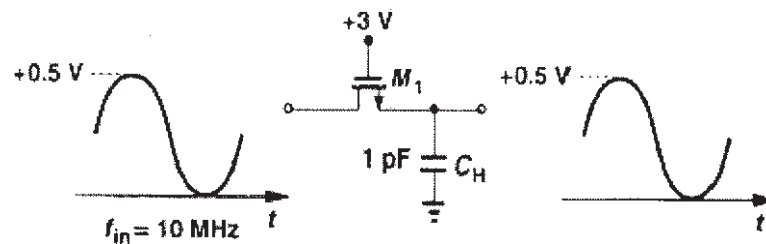- Q3) a)** In the circuit shown in figure calculate the minimum and maximum on-resistance of M_1 . Assume $\mu_n C_{ox} = 50 \mu A/V^2$, $W/L = 10/1$, $\gamma = 0$, $V_{TH} = 0.7 V$ and $V_{DD} = 3V$. [4]



- b) Draw and Explain following analog CMOS circuits [4]
- LNA
 - Mixer
 - DAC
 - Tuned Amplifiers
- c) What is source degeneration ? Explain the effect degeneration resistance on the voltage gain of CS amplifier. [2]

- Q4) a)** Design a fully differential telescopic op-amp with the following specifications: [4]

$V_{DD} = 3\text{ V}$, differential output swing = 3V, power dissipation = 10mW, voltage gain = 2000. Assume $\mu_n C_{ox} = 60\mu\text{A/V}^2$, $\mu_p C_{ox} = 30\mu\text{A/V}^2$, $\lambda_n = 0.1\text{V}^{-1}$, $\lambda_p = 0.2\text{V}^{-1}$ (for an effective channel length of 0.5 μm) $\gamma = 0$, $V_{THN} = |V_{THP}| = 0.7\text{ V}$.

- b) What is the necessity of MOS diode/active resistor? Draw the MOS diode/active resistor circuits for NMOS and PMOS transistors. Is there any difference in gain of the following amplifier circuits, [4]

- i) Common source amplifier with NMOS diode connected load
- ii) Common source amplifier with PMOS diode connected load

Justify your answer with the suitable circuit diagrams.

- c) With the help of detailed equivalent circuit diagram explain the parasitic capacitances and resistances involved in a MOSFET. [2]


- Q5) a)** What is the principle of operation of Current mirrors? Explain in short nonideal effects of current mirrors. What is the use of current mirrors?[4]

- b) What is difference between active mixer and passive mixers. Draw and explain the architectures of both the mixers. [4]

- c) A 1 V peak-to-peak sinusoidal signal is applied to an 10-bit DAC which has a V_{ref} of 5 V. Find the maximum SNR of the digitized analog output signal. [2]

- Q6) a)** Draw the small signal model MOS transistor including all the parasitic capacitances and derive the equation for its transconductance (g_m) and transition frequency (f_T). [4]

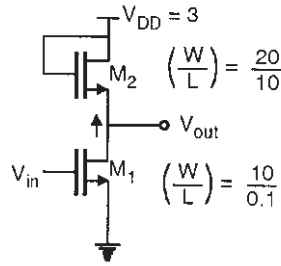- b) Determine the voltage gain of the circuit shown in Figure If $I_{D1} = I_{D2} = 1$ mA, $\lambda = 0.1$, $\mu_n C_{ox} = 100 \mu\text{A/V}^2$. Neglect body effect. [4]



- c) For an ideal n channel MOSFET with parameters $L = 1.25 \mu\text{m}$, $\mu_n = 650 \text{ cm}^2/\text{Vs}$, $C_{ox} = 6.9 \times 10^{-8} \text{ F/cm}^2$, $V_{THn} = 0.65 \text{ V}$. Design the channel width W such that $I_{DSSAT} = 4 \text{ mA}$ with $V_{GS} = 5 \text{ V}$. [2]

Q7) a) Write Short notes on following(Any Two) : [4]

- i) DAC Topologies in CMOS ICs
- ii) Techniques used in Micro power opamp
- iii) Non-Idealities in MOSFET

- b) Design an NMOS cascode current source for an output impedance of $500 \text{ k}\Omega$ and a current of 0.5 mA . Assume M_1 and M_2 are identical


$$\mu_n C_{ox} = 100 \mu\text{A} \text{ and } \lambda = 0.1 \text{ V}^{-1}. \quad [4]$$

- c) If the sampled analog input applied to an 8 bit SAR converter is $0.7 V_{ref}$. Find the output digital word. [2]

Q8) a) Write Short notes on following(Any Two) : [4]

- i) High Speed Opamp
- ii) Bandgap Reference Source
- iii) CMOS Inverter as an amplifier

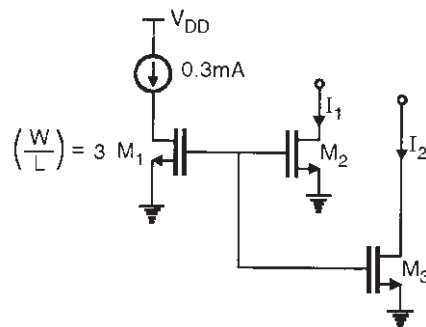- b) Design a current mirror circuit that produces a currents $I_1 = 0.2 \text{ mA}$ and $I_2 = 0.5 \text{ mA}$ from a reference current source of 0.3 mA connected to transistor with aspect ratio 3. [4]



- c) Define and derive expressions for, [2]
- g_m ,
 - g_{mb} .

