

Total No. of Questions : 6]

SEAT No. :

**P23**

[Total No. of Pages : 2

**APR - 18/TE/Insem. - 25**

**T.E. (E&TC)**

**POWER ELECTRONICS**

**(2012 Revised Course) (Semester - II)**

*Time : 1 Hour]*

*[Max. Marks : 30*

*Instructions to the candidates:*

- 1) *Answer any three questions.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right side indicate full marks.*
- 4) *All questions carry equal marks.*
- 5) *You are advised to attempt not more than 3 questions.*
- 6) *Use of logarithmic tables slide rule, Mollier charts, electronic pocket calculator and steam tables in allowed.*
- 7) *Assume suitable data, if necessary.*

**Q1)** a) What is two transistor analogy? Explain. Derive an expression for its Anode current  $I_A$ . [6]

b) Draw construction diagram of n-channel enhancement type MOSFET with its steady state characteristics. [4]

OR

**Q2)** a) What is IGBT? Explain its characteristics. [4]

b) What is the need of triggering Circuits in Power Circuits? Explain with circuit diagram & waveforms working of UJT based SCR firing circuit. [6]

**Q3)** a) What are phase controlled converters? Explain with circuit diagram & waveforms working of  $1\phi$  Half controlled converter with RL load. Comment on pf & its improvement technique. [6]

b) A single phase semiconverter is operated from 120V, 50Hz AC supply. The load resistance is  $10\Omega$ . If the average o/p voltage is 25% of the maximum possible average output voltage. [4]

- Determine
- i) firing angle  $\alpha$
  - ii) Rms & Average output current

OR

**P.T.O.**

**Q4) a)** Draw & explain with circuit diagram & waveforms working of single phase fully controlled converter with RL load. Comment on p.f. [6]

b) A single phase fully controlled converter supplies an inductive load. Assume o/p current is constant & is equal to  $I_{dc}$ . Determine the following performance parameters if the supply voltage is 230V & firing angle is  $\frac{\pi}{6}$ . [4]

i) Average o/p voltage

ii) Fundamental p.f.

iii) Supply p.f.

**Q5) a)** What are DC to AC Converters? Explain with circuit diagram & waveforms working of 1 $\phi$  full bridge MOSFET based VSI with R load. [6]

b) Compare 120° & 180° modes of conduction of 3 $\phi$  Voltage Source Inverter(VSI). [4]

OR

**Q6) a)** What is the need of 3 $\phi$  VSI in industry? Explain with circuit diagram & waveforms working of 3 $\phi$  VSI with R-load. [6]

b) Explain working of 1 $\phi$  Half bridge Inverter with RL load. [4]

