

Total No. of Questions : 8]

SEAT No. :

P3763

[Total No. of Pages : 2

[4960] - 1256

M.E. (E & TC) (VLSI & Embedded Systems)

Analog CMOS DESIGN

(2013Pattern) (Semester - II)

Time : 3 Hours]

[Max. Marks : 50

Instructions to the candidates:

- 1) *Answer any five questions.*
- 2) *Neat diagrams must be drawn wherever necessary.*
- 3) *Figures to the right indicate full marks.*

- Q1)** a) Explain with suitable diagrams N-channel transistor as a switch. [5]
b) With the help of suitable schematic & necessary expressions, explain current source inverter. [5]
- Q2)** a) Explain current & voltage references with neat circuit diagram. Derive the expression for reference voltage. [5]
b) What are the different types of inverting CMOS amplifier. Explain Push-Pull inverter with neat circuit diagram. [5]
- Q3)** a) What are the advantages of cascode amplifier over the inverting amplifier. Explain simple cascode amplifier with neat circuit diagram. [4]
b) Carry out small signal analysis of CMOS differential amplifier & find out r_{out} , A_v , CMRR and V_{out} . [4]
c) What is the role of slew rate and noise in CMOS differential amplifier. [2]
- Q4)** a) Explain Class A Amplifier with suitable circuit diagram & waveforms. Derive the equations of r_{out} , I_{out}^- & I_{out}^+ . [4]

P.T.O.

- b) Explain push-pull common source amplifier with neat circuit diagram. [4]
- c) What are the main objectives of output Amplifier? [2]
- Q5)** a) Explain DAC with suitable diagram & input - output characteristics. Derive the equation of ENOB. [4]
- b) Explain analysis method for switched capacitors circuits using two phase nonoverlapping clocks. [4]
- c) What is tuned amplifiers? Explain. [2]
- Q6)** a) Explain zero as bandwidth enhancer. Give the expression for bandwidth. [4]
- b) Explain the neutralization & unilateralization with suitable circuit diagrams. [4]
- c) Differentiate the method of open-circuit time constant and the method of short circuit time constants. [2]
- Q7)** a) Explain LNA topologies power match versus noise match with suitable circuit diagrams & necessary equations. [4]
- b) Explain differential LNA with neat circuit diagram. [4]
- c) What is role of single balanced mixer in LNA? [2]
- Q8)** a) Explain active double balanced mixer with neat circuits. [4]
- b) How nonlinear systems works as linear mixers? Explain square-law MOSFET mixer with neat circuits. [4]
- c) Define linearity & isolation w.r.t. mixer. [2]

