

Total No. of Questions : 8]

SEAT No. :

P1485

[Total No. of Pages : 2

[6002]-112

S.E. (Electronics/ E&T.C)

ELECTRONIC CIRCUITS.

(2019 Pattern) (Semester-III) (204181)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Figure to the right indicate full marks.
- 3) Neat diagrams must be drawn wherever necessary.
- 4) Assume suitable additional data, if necessary.
- 5) Use of non-programmable calculator is allowed.

- Q1)** a) Draw block diagram of regulated power supply and explain the function of each block? [6]
b) With the help of neat diagram explain buck-boost converter? [6]
c) Draw and explain low dropout regulator? [6]

OR

- Q2)** a) Design a regulated power supply using LM 317 for output voltage $9V$ and $15V$ $I_{Adj}=100\mu A$. [6]
b) Explain the working of SMPS with neat diagram? [6]
c) Compare regulated and unregulated power supply? [6]

- Q3)** a) List all parameter's of op-amp. Explain any four in brief ? [6]
b) Explain significance of negative feed back, in op-amp amplifier? [5]
c) A dual input balanced output differential amplifier has following specification $R_c=2.7K\Omega$, $R_E=4.5k\Omega$, $\pm V_{CC}=\pm 10V$, $\beta=100$; $V_{BE}=0.7V$; $r_e=26.34\Omega$ calculate [6]
i) Voltage gain (A_d)
ii) R_{in}
iii) R_o

OR

- Q4)** a) Draw block diagram of op-amp and explain each block? [6]
b) Compare inverting and non-inverting configuration of op-amp with following parameters:
i) Feedback Type
ii) R_i
iii) Gain
iv) Bandwidth [5]

P.T.O.

- c) Determine the Q point for dual input and balanced output differential amplifier with $R_C=R_E=65K\Omega$ and supply voltage $\pm 15V$ assume suitable data. [6]

- Q5)** a) Draw an inverting summing amplifier with three input and derive expression for the output voltage $V_o = -(V_a + V_b + V_c)$ [6]
 b) Design a practical Integrator with input Signal of 1.5 vpp and cut off frequency of 3KHz for DC voltage gain of 10. [6]
 c) Draw circuit diagram of 30p-amp Instrumentation amplifier and write its o/p equation? [6]

OR

- Q6)** a) With the help of neat diagram explain working of symmetrical schmitt trigger? [6]
 b) Design a square wave generater using op-amp for frequency 1KHz to 10 KHz with 50 % duty cycle. draw diagram with component value. [6]
 c) Explain practical differentiator circuit with neat diagram? list limitations of ideal differentiator? [6]
- Q7)** a) Explain voltage to current converter with floating load? [6]
 b) Determine the output voltage produced by 4 bit R-2R ladder DAC with $V_{ref}=5v$ for bit sequence i) 0110 ii) 1101 [5]
 c) Explain working of flash ADC in details. [6]

OR

- Q8)** a) Define terms. [6]
 i) Lock range
 ii) Capture range.
 iii) Pull in time
 iv) Free running frequency.
 b) With the neat diagram explain working of weighted resistor DAC? [6]
 c) Find the digital output of an ADC having $t_1=83.33$ Msec and $V_R=100$ mv for an input voltage. of +100mV. The clock frequency is kHz [5]

