

Total No. of Questions : 8]

SEAT No. :

P3512

[4858]-1048

[Total No. of Pages : 2

T.E. (E & TC) (Semester - II)

POWER ELECTRONICS

(2012 Pattern) (End Sem.)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Neat diagrams must be drawn wherever necessary.
- 2) Figures to the right indicate full marks.
- 3) Your answers will be valued as a whole.
- 4) Use of logarithmic tables slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.
- 5) Assume suitable data, if necessary.

- Q1)** a) What are phase controlled converter? Explain with circuit diagram working of 1ϕ Half controlled converter with suitable load. Draw suitable waveforms & comment on p.f. [7]
- b) What is inverter? Explain with diagram 3ϕ voltage controlled inverter with star load (R). Comment on waveforms & Duty cycle. [7]
- c) What is IGBT? Explain with characteristics. [6]

OR

- Q2)** a) What is the need of dual converters in the industries? Explain with diagram & waveforms, working of 1ϕ dual converter with highly inductive load. [7]
- b) Explain with circuit diagram & waveforms working of 1ϕ Full controlled converter with RL load? Justify what is Inversion & Rectification mode with waveforms. [7]
- c) What is bridge Inverter? Explain with circuit diagram & waveforms. [6]

- Q3)** a) What are DC-to-DC converters? Explain with circuit diagram & waveforms working of 4 Quadrant chopper? State its applications. [9]
- b) What is AC to AC controller? Explain with circuit diagram working of 1ϕ AC full wave AC to AC controller with balanced star Load (R) [9]

OR

P.T.O.

- Q4) a) i)** What is chopper? Explain in brief.
- ii)** A DC chopper has a resistance of 10Ω & input voltage is 220V. When the chopper switch remains ON its voltage drops to 2V. & chopping frequency is 1KHz. If the Duty cycle is 50% Determine,
- 1) Average o/p volt
 - 2) Rms o/p voltage
 - 3) Chopper freq
 - 4) Input resistance of chopper **[10]**
- b)** Explain with circuit diagram & waveforms working of triac based AC power controller ckt. Comment on p.f. Justify why SCR based controllers are preferred over triac based controllers. **[8]**

- Q5) a)** Explain with block schematic working of off-line UPS. State its specifications & applications. **[8]**
- b)** What are speed control techniques of DC Motors? Explain with circuit diagram working of 1ϕ separately Excited DC Motor with Inductive Load. Comment on p.f. **[8]**

OR

- Q6) a)** Compare ON-Line UPS with Off-Line UPS. Justify why ON-Line is better than Off-Line with technical reasons. **[8]**
- b)** Write short notes on : **[8]**
- i) Battery charger
 - ii) Electronic Ballast

- Q7) a)** What are resonant converters? Explain with circuit diagram & waveform working of ZVS? **[8]**
- b)** A Snubber circuit is used in SCR circuit for protection of di/dt , dv/dt . The value of RLC being 4Ω , $6\mu H$, & $6\mu F$ respectively & Supply being 400V. Find the maximum permissible value of dv/dt . Assume the load resistance to be 10Ω . **[8]**

OR

- Q8) a)** Compare Linear, switched mode & Resonant converter based power supplies. **[6]**
- b)** Write short notes on : **[10]**
- i) HVDC
 - ii) Induction Heating
 - iii) Protection circuits

