

S.E. (E & TC / Electronics)

NETWORK THEORY

(2012 Course) (Semester - I) (204183)


Time : 2 Hours]

[Max. Marks : 50]

Instructions to the candidates:

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6 and Q.7 or Q.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Assume suitable data, if necessary.

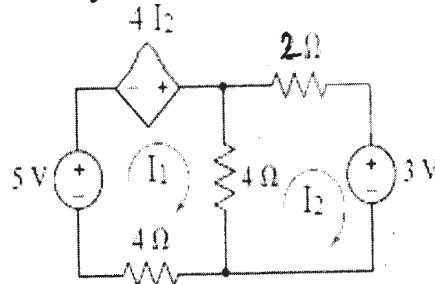Q1) a) Apply mesh analysis and determine the currents I_1 and I_2 . [6]




b) Explain the following terms with example: [6]

- i) Oriented graph.
- ii) Tieset matrix.
- iii) f-cutset matrix.

OR


Q2) a) Consider the circuit given below: [6]

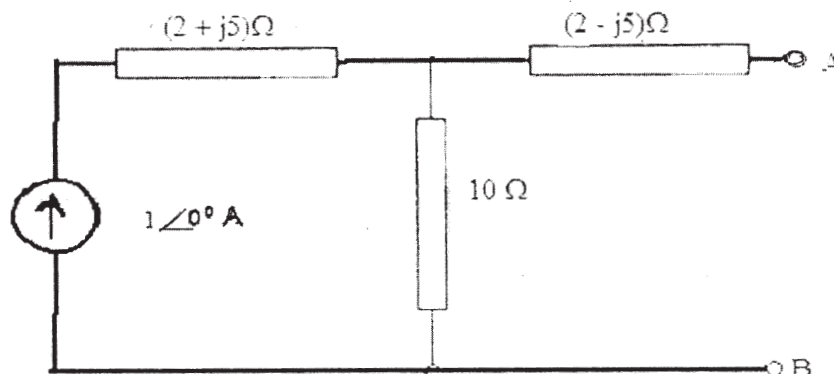- i) Obtain Thevenin's equivalent circuit.
- ii) What load should be connected between terminals A-B for maximum power- transfer to the load?
- iii) Calculate the maximum power transferred to the load.




P.T.O.

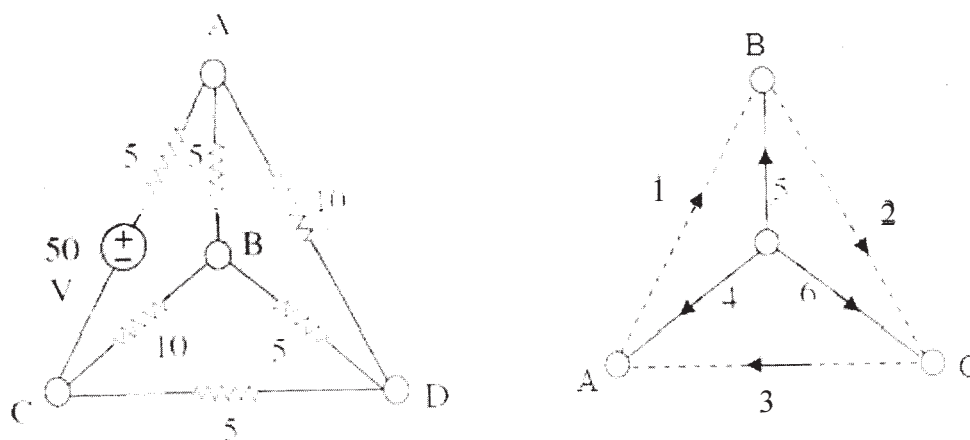- b) For the circuit and its graph shown below: [6]
- Write a tie-set schedule for the tree [4, 5, 6].
 - Find the branch-impedance matrix.
 - Obtain the loop impedance matrix.



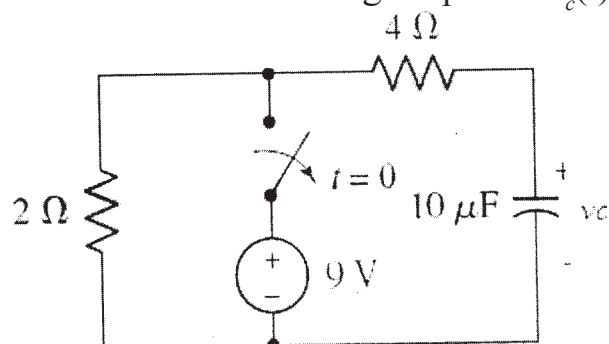- Q3) a) For the circuit shown below, find the voltage v_c at $t = 200 \mu s$. Find the expression for the current through capacitor $i_c(t)$ [6]




- b) Define the term Quality factor.

Prove for a series RLC resonant circuit $f_0 = \sqrt{f_1 f_2}$. [6]

OR

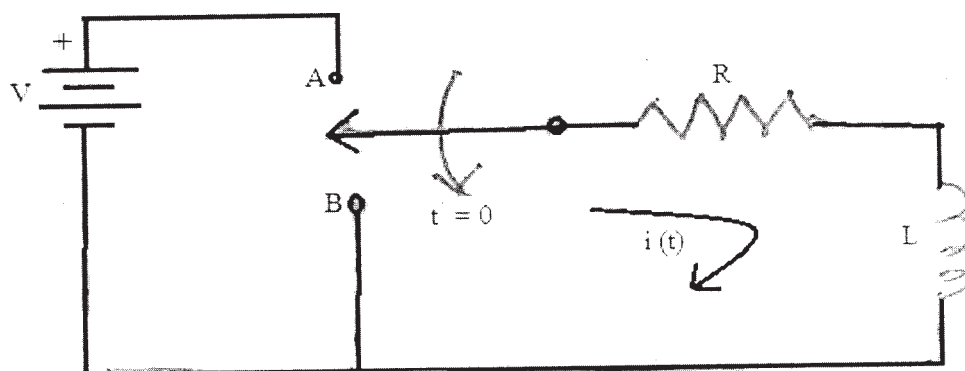- Q4) a) Derive the expression for the current $i(t)$ for the series RL circuit shown below. [6]




- b) A series resonant circuit has a bandwidth of 100Hz and contains a 20 mH inductance and a $20 \mu\text{F}$ capacitance. Determine: [6]
- f_0
 - Q_0 and
 - Impedance Z at resonance.

- Q5)** a) For any symmetrical network, prove that the characteristics impedance Z_0 is the geometric-mean of open & short circuit impedances. [6]
- b) Design a constant-k T-type low pass filter with following specifications:
Design resistance $R_0 = 560 \Omega$ and cut-off frequency $f_c = 2\text{KHz}$.
Also determine the frequency at which the attenuation offered by the filter is 17.372dB. [7]

OR

- Q6)** a) Design a symmetrical π attenuator with following specifications:
Attenuation = 6dB and characteristic resistance of 6 dB.
Draw a neat diagram of the properly terminated attenuator showing the component values. [6]
- b) Answer the following: [7]
- State the limitations of prototype filters.
 - Explain how these limitations are overcome using m-derived filters.
 - Draw the block diagram of composite filters.
 - Advantages of composite filters.

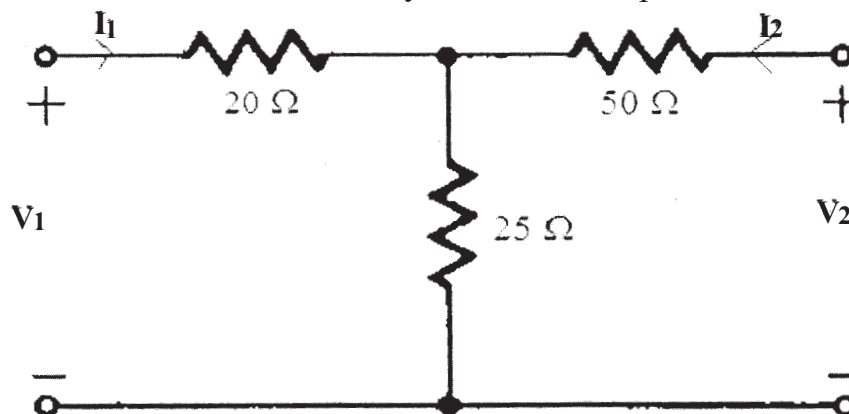
- Q7)** a) Find z-parameters for the two-port network shown below. [6]
- State whether the network is symmetrical/reciprocal.



b) Consider the RC network shown below.


[7]

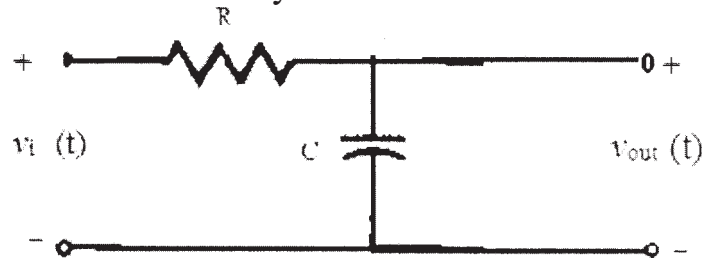- i) Draw the s-domain equivalent circuit.
- ii) Find the transfer function $H(s) = \frac{V_{out}(s)}{V_i(s)}$.
- iii) Find the poles and zeros of the function $H(s)$ and
- iv) State whether the system is stable or not.



OR

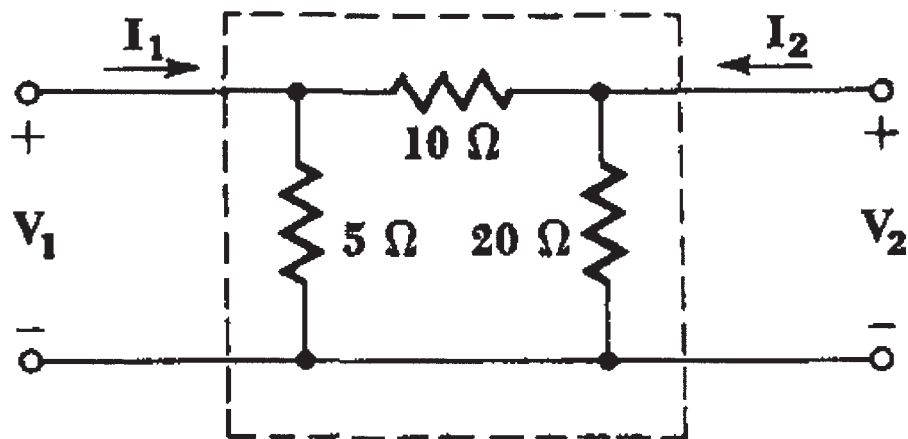- Q8)** a) Find the four short circuit admittance parameters for the resistive two port network. Determine whether the network is symmetrical/reciprocal. [6]



b) State and explain:

[7]

- i) Driving point functions for one port networks.
- ii) Driving point and transfer functions for two port networks.

