

Total No. of Questions : 8]

SEAT No. :

PB3622

[6261]-27

[Total No. of Pages : 2

S.E. (E & TC/Electronics/Computer Engineering)

DIGITAL CIRCUITS

(2019 Pattern) (Semester - III) (204182)

Time : 2½ Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer Q. No.1 or Q.No.2, Q.No.3 or Q.No.4, Q.No.5 or Q.No.6 and Q.No.7 or Q.No.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Use of Calculator is allowed.
- 5) Assume Suitable data, if necessary.

- Q1)** a) Explain implementation of full adder using 8 : 1 MUX. [6]
b) Explain 3-bit parity checker circuit. [6]
c) Implement 1 : 16 demux using 1 : 4 demux. [6]

OR

- Q2)** a) Implement the given logic function using a 4 : 1 multiplexer. [6]
$$f(A, B, C) = \sum m(0, 1, 2, 4, 7)$$

b) Implement 3-bit parity generator circuit. [6]
c) Explain the working of a half-subtractor? Draw its logic diagram. [6]

- Q3)** a) Design a circuit to generate the following sequence using D FFs 1011. [8]
b) Explain with neat diagram the types of shift register. [9]

OR

- Q4)** a) Design a 3- Bit asynchronous counter using JK FF. [9]
b) Convert SR flip - flop into JK flip flop. [8]

- Q5)** a) Write short note on state diagram and state table with suitable example. [6]
b) Write short note on Principal Component of an ASM Chart. [6]
c) Draw the state diagram of SR flip flop and JK flip flop. [6]

OR

P.T.O.

- Q6)** a) Draw ASM chart for 2 bit binary counter having enable line E Such that :
E = 1, Count Enable and E = 0, Count Disable. [9]
b) Compare Mealy and Moore machine. [9]

- Q7)** a) Classify and explain the characteristics of memories. [9]
b) Implement 3-bit binary to Gray code converter using PROM. [8]

OR

- Q8)** a) Design and implement 2-bit comparator using PAL? [9]
b) Explain CPLD architecture. [8]

* * *