

[Total No. of Questions: 12]

S.E. (E&TC/ Electronics)
DIGITAL ELECTRONICS
(204185) (2012 Course)

Time : 2 Hours]

[Max. Marks : 50

Instructions to the candidates:

- 1) Attempt Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8, Q.9 or Q.10, Q.11 or Q.12 .*
- 2) Neat diagrams must be drawn wherever necessary.*
- 3) Figures to the right indicate full marks.*
- 4) Assume suitable data, if necessary.*
- 5) Use of logarithmic tables, slide rule and electronic non programmable calculator is allowed.*

- Q1** a. Explain following characteristics of digital ICs
1. Noise margin
2. Fan in & Fan out **02**
- b Simplify and implement following expression using K-map.
- $Y = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$ **04**
- OR**
- Q2** a Draw CMOS circuit for NOR gate. **02**
- Design and implement following function using 4:1 multiplexer
- $F = \sum m(1, 3, 4, 5)$ **04**
- Q3** a Draw and explain TTL to CMOS interface. **04**
- b What do you mean by multiplexure tree? Explain. **02**
- OR**
- Q4** a Give comparisons between TTL, ECL and CMOS logic families. **04**


- b What do you mean by priority encoder? 02
- Q5** a Draw and explain SR Flip Flop using NAND gates. 02
- b Convert D to T flipflop 04

OR

- Q6** a What is clock skew and clock jittering in synchronous circuits? 02
- b Design a mod-6 synchronous counter. 04
- Q7** a Compare Mealy machine with Moore machines. 02
- b Design a sequence detector to detect the sequence 110, using JK flip-flops. Use Mealy Machine 04

OR

- Q8** Reduce following state diagram

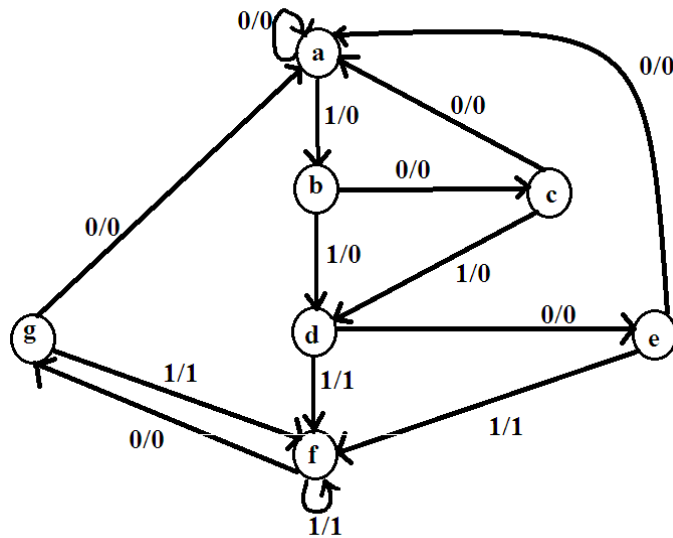

- Q9** a Draw and explain CPLD with it's block diagram. 06
- b Design seven-segment decoder using PLA. 07

OR

- Q10** a Differentiate between static and dynamic RAM? 04
- b Compare between different types of PLDs. 03

- c Implement following function using PLA
 $F_1(A, B, C) = \sum M(0, 2, 5, 7)$
 $F_2(A, B, C) = \sum M(2, 3, 4, 5)$ **06**
- Q11** a Differentiate between signals and variables. **04**
- b What is a structural type of modeling? Explain with an example **04**
- c Write VHDL code for 3:8 decoder using case statement **05**
- OR**
- Q12** a Explain architecture with different modeling styles. **06**
- b Explain the difference between concurrent and sequential statements. **04**
- c Explain loop statement with example. **03**

❌ ❌ ❌