

Total No. of Questions : 8]

SEAT No. :

P4016

[Total No. of Pages : 2

[5155] - 264

M.E. (E&TC) (VLSI & Embedded Systems)

FAULT TOLERANT SYSTEMS

(2013 Credit Pattern)

Time : 3 Hours]

[Max. Marks : 50

Instructions to candidate :

- 1) Neat diagrams must be drawn wherever necessary.
- 2) Assume suitable data, if necessary.
- 3) Solve any five questions.

Q1) a) Define

- i) Cube
- ii) Primitive cube.

What is the procedure of constructing a cube?

[5]

- b) Construct a binary decision diagram for a JK flip-flop with asynchronous set (S) & reset (R) inputs. [5]

Q2) a) Briefly explain following types of cross point faults. [8]

- i) Shrinkage fault
- ii) Growth fault
- iii) Appearance fault
- iv) Disappearance fault.

- b) Discuss the term pin-fault model. [2]


Q3) a) Explain following terms : [4]

- i) Stuck RTL variables
- ii) Fault variables

- b) Describe the working of self checking checkers. [6]

P.T.O.

 - Q4) a)** Define bridging fault. Find test vector that determine the OR bridging fault between input A & B in the following figure (Figure 1). [4]



- b) Explain how testing is performed using test-response compression technique. Draw a suitable diagram. [6]
- Q5) a)** How to detect hazards present in asynchronous circuits? [6]
- b) List any four benefits of on-line testing. [4]
- Q6) a)** With the help of suitable diagram explain the triple modular redundancy (TMR) technique used in fault tolerant design. [5]
- b) Discuss the functional & structural forms of off-line BIST techniques. [5]
- Q7) a)** Draw & explain chip architecture for IEEE 1149.1. [8]
- b) Briefly explain exhaustive form of testing. [2]
- Q8) a)** Write a short note on syndrome testing. [6]
- b) Define following terms : [4]
- i) Structural faults
 - ii) Functional faults

▽▽▽▽