

[5155] - 261

M.E. (E&amp;Tc) (VLSI &amp; Embedded System Design)

ANALOG CMOS DESIGN

(2013 Pattern) (Semester - II)

Time : 3 Hour]

[Max. Marks : 50

Instructions to the candidates :

- 1) Answer any Five questions.
- 2) Figures to the right indicate full marks.
- 3) Use of electronic pocket calculators is allowed.
- 4) Assume suitable data, if necessary.

**Q1)** a) Discuss the effect of channel length modulation and body effect on MOSFET and show how these are taken care of in small signal equivalent model. [5]

- b) For the circuit of CS amplifier with diode connected load as shown in Fig. 1, calculate small signal voltage gain if  $(W/L)_1 = 50/0.5$ ,  $(W/L)_2 = 10/0.5$  and  $I_{D1} = 0.5$  mA. Assume  $\mu_n C_{ox} = 2\mu_p C_{ox} = 60$   $\mu A/V^2$ . Also find voltage gain if  $M_2$  is PMOS. Neglect second order effects. [5]

 


Figure 1

- Q2)** a) With the help of suitable schematic and expressions, explain MOSFET as a switch, diode and active resistor. [5]
- b) What is band gap reference circuit, draw any one band gap voltage or current reference circuit and explain the same. [5]

P.T.O.

- Q3) a)** List and elaborate the important performance parameters of CMOS operational amplifier. [5]
- b) Draw cascode amplifier with current source load and list its advantages and limitations over single stage CS and CG amplifier. [5]

- Q4) a)** Determine the differential and common mode voltage gain of the circuit shown in Fig 2. Assume  $\lambda \neq 0$ , also  $M_1$  and  $M_2$  are identical and  $M_3$  and  $M_4$  also. Also find CMRR. assume non ideal tail current source with internal resistance  $R_{ss}$ . [5]

 


Figure 2

- b) Draw circuit diagram of two stage CMOS op amp and explain its working. [5]
- Q5) a)** List and elaborate static characteristics of Digital-to-Analog converter. [4]
- b) How zeros work as bandwidth enhancers, give expression of bandwidth of such circuit. [4]
- c) What is effect of source degeneration resistance on the voltage gain of CS amplifier? [2]
- Q6) a)** Write short notes on [6]
- Tuned amplifiers
  - DAC topologies in CMOS monolithic circuits
  - High speed op amps
- b) Explain in detail open and short circuit techniques for bandwidth estimation. [4]

- Q7)** a) What is difference between active and passive mixers. Draw' and explain their architectures. [5]
- b) List and elaborate the design considerations for RF chip. [5]
- Q8)** a) Draw circuit diagram of differential LNA and explain how it overcomes drawbacks of single ended LNA. [5]
- b) With the help of different Low Noise Amplifier (LNA) topologies explain how noise and power trade off is achieved. [5]

▽▽▽▽